

Fig. 3.EM14(vi)

The initial increase of Q with frequency f is due to the fact that the inductive reactance increases linearly with f while the resistance due to the skin effect does not rise faster than $f^{1/2}$. At high frequencies, the dielectric losses in the coil form and the insulating material used are greater than the losses due to skin effect. As the resistance due to dielectric losses rises with frequency as f^3 , the Q falls at high frequencies. At intermediate frequencies, the increase of the resistance R due to skin effect and dielectric losses is such that $Q(\omega L/R)$ remains almost constant.

24. Which element—an inductor or a capacitor—does possess a higher Q at a given frequency?

Ans. Capacitor, because the losses in a capacitor are much smaller.

25. Is the coil resistance r the same at all frequencies?

Ans. No. At low frequencies, r is the dc resistance of the wire of the coil. As frequency increases, in the radio frequency range, r increases owing to the skin effect, eddy current losses, and dielectric losses in the coil form. If the core is ferromagnetic, hysteresis losses will also enhance r .

26. How can you reduce the eddy current for a magnetic core?

Ans. By laminating the core or using a ferrite core.

[See also the 'Aids to the Viva Voce' for Expt. No. EM12 and EM13 and the questions on electronic meters at the end of Part 2.]

Study of response curve of a series LCR circuit and

Experiment No. EM15

INVESTIGATIONS ON A SERIES RESONANT CIRCUIT

determination of its resonant frequency, impedance at resonance

Object : quality factor and band width

1. To draw the resonance curve of a series LCR circuit for various values of R and L/C , and to find the Q factor in each case.
2. To find the Q factor from the ratio V_c/V_i at resonance, where V_c and V_i are the capacitor voltage and the source voltage, respectively.
3. To draw the phasor diagram of voltages at series resonance.

Theory :

In Fig 3.EM15(i), a coil of self inductance L and resistance R_L is connected in series with an external resistance r , and a capacitance C . The total resistance in the circuit is $R = R_s + R_L + r$, where R_s is the internal resistance of the ac voltage source. This circuit is known as the series LCR circuit. If V_i is the driving voltage, a current I will flow in the circuit. At an angular frequency ω of the ac source, the magnitude of the current is

$$I = \frac{V_i}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \quad \dots (i)$$

As the frequency $f = \frac{\omega}{2\pi}$ is increased, the current at first increases, attains a maximum, and then falls, as shown in Fig. 3.EM15(ii). 2

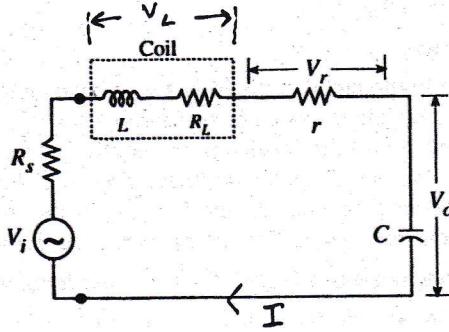


Fig. 3.EM15(i) 1

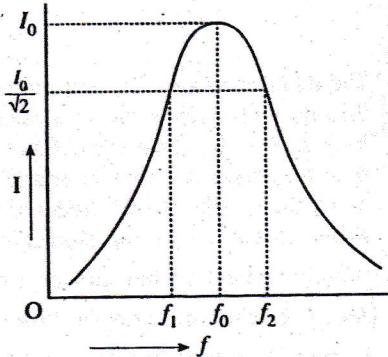


Fig. 3.EM15(ii) 2

The I versus f curve [Fig. 3.EM15(ii)] is known as the *resonance curve*. The maximum current I_0 is obtained at a frequency f_0 , called the series resonant frequency. It is given by

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} \quad \dots (ii)$$

At resonance, the current I is in phase with the voltage V_i . The Q factor of the circuit is

$$Q = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \dots (iii)$$

The Q factor denotes the sharpness of resonance. The higher the Q , the sharper the fall of I on either side of resonance. Let the frequencies where the current drops to $I_0/\sqrt{2} = 0.707I_0$ be f_1 and f_2 . The bandwidth of the circuit is $(f_2 - f_1)$ and the Q factor can be written as

$$Q = \frac{f_0}{f_2 - f_1} \quad \dots (iv)$$

Equation (iii) shows that Q depends on R and L/C . As R decreases, Q as well as the peak current at resonance $I_0 (= V_i/R)$ increases, as shown in Fig. 3.EM15(iii). For a fixed R , if L/C increases, Q also increases, but I_0 remains fixed [Fig. 3.EM15(iv)].

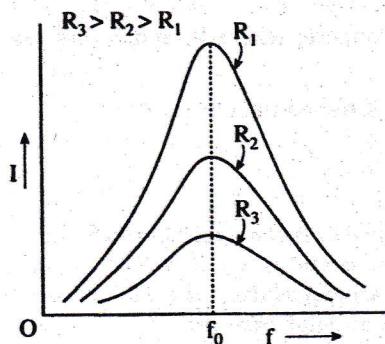


Fig. 3.EM15(iii) 3

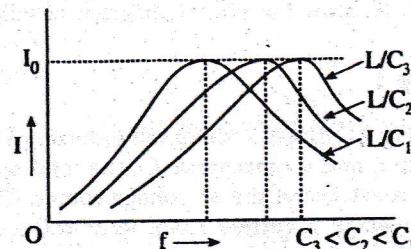


Fig. 3.EM15(iv) 4

For a give
The capaci

Thus Q ca

Let V'_i be
At resonance, I
 r , we have $V_r =$
phasors $V_r, V'_i,$
the voltages V_C
in series).

Apparatus

- (i) An ac source of 100 V, 50 Hz.
- mH, $R_L = 10\Omega$
- (iv) three resistors R_1, R_2, R_3

Procedure

1. Use the circuit as it is.
2. Switch on the power supply so that V_i is the applied voltage. Disconnect the inductor L from the rest of the circuit.
3. At different frequencies, measure the current I from the relay.
4. Plot I versus f for different values of L/C and R . Calculate the peak current I_0 and the peak frequency f_0 for each case. Calculate the bandwidth $(f_2 - f_1)$. Calculate the Q factor for each case.
5. Set the inductor L and the capacitor C separately. Calculate the peak current I_0 and the peak frequency f_0 for each case.
6. Repeat the experiment for different values of R .

For a given L , L/C can be increased by taking smaller values of C .

The capacitor voltage at resonance is given by

$$V_c = QV_i.$$

... (v)

num, and then

not required now

in current I_o is

cuit is

the fall of I on
be f_1 and f_2

peak current
eases, Q also
 $\propto C_3$
 $\propto C_2$
 $\propto C_1$
 $\propto C_1$

Thus Q can also be found from the ratio V_c/V_i at resonance.

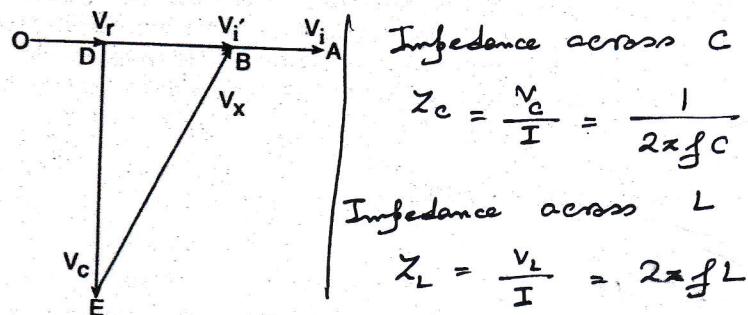


Fig. 3.EM15(v)

Let V'_i be the voltage at resonance across the resonant circuit when it is connected to the source. At resonance, I and V_i are in phase. So, $V'_i (= V_i - IR_s)$ is in phase with V_i . If V_r is the voltage drop across r , we have $V_r = Ir$, so that V_r is also in phase with V_i . Let the straight lines OA, OB, and OD denote the phasors V_i , V'_i , and V_r respectively [Fig. 3.EM15(v)]. The phasor DB then represents the phasor sum of the voltages V_c ($\equiv DE$) and V_x ($\equiv EB$), V_x being the voltage drop across the coil (consisting of L and R_L in series).

Apparatus and Accessories :

- (i) An audio oscillator (of output resistance $R_s \approx 10$ ohm), (ii) the given coil (typically $L \approx 10$ mH, $R_L = 100$ ohm or less), (iii) three capacitors (typically 0.05, 0.1 and 0.15 μF), (iv) three resistances (typically 30, 50 and 70 ohm), and (v) an electronic voltmeter (EVM).

Procedure :

1. Use the minimum value of C ($\approx 0.05 \mu\text{F} = C_1$) and a resistance r (say, 30 ohm = r_1). Set up the circuit as in Fig. 3.EM15(i). Here $R = R_1 = R_s + R_L + r_1$.
2. Switch on the ac source and set its output voltage V_i to a convenient value (say, 3V rms). Note that V_i is the open-circuit voltage across the source terminals, i.e. the voltage with the network disconnected. Keep V_i constant as the frequency is varied.
3. At different frequencies measure the voltage V_r across r by the EVM, and calculate the current I from the relationship $I = V_r/r$.
4. Plot I against the frequency f . From the plot, find the resonant frequency f_o and the bandwidth ($f_2 - f_1$). Calculate Q from Eq. (iv).
5. Set the oscillator frequency at the resonant frequency f_o and measure the voltage V_c across the capacitor. Calculate Q from Eq. (v) and compare it with the value determined in step 4.
6. Repeat steps 2 to 5 for two other values of r (say, $r_2 = 50\Omega$, and $r_3 = 70\Omega$).

7. Keep r fixed at its minimum value (≈ 30 ohm) and repeat steps 2 to 5 for two other values of C (say, $C_2 = 0.1 \mu\text{F}$ and $C_3 = 0.15 \mu\text{F}$).

8. At resonance, draw the phasor diagram [Fig. 3.EM15(v)] by, first drawing, to a chosen scale the straight line OA representing V_i . From OA, cut off the segment OB to represent V_r' , and the segment OD to represent V_r . With centre at D, draw a circular arc of radius representing V_c . With centre at B, draw another circular arc of radius corresponding to V_x . Let the two arcs intersect at E. Then DE and EB will represent V_c and V_x , respectively. (Note that the capacitor voltage lags the current, and so the arcs must be drawn on the lower side of OA.) Measure $\angle BDE$ and $\angle DBE$. Since the capacitor losses are negligible, $\angle BDE$ is expected to be nearly 90° , showing the 90° phase lead of the current over V_r . However, inductors are imperfect and so $\angle DBE$ will be less than 90° , reflecting that the voltage across the coil leads the current by less than 90° .

Experimental Results :

TABLE 1
Data for the resonance curve

1A. $C = \dots \mu\text{F} (= C_1)$, $r = \dots \Omega (= r_1)$.

Source frequency f (Hz)	Input voltage V_i (volt)	Voltage across r V_r (volt)	Current I (= V_r/r) (A)
...
...
...
etc.	etc.	etc.	etc.

Make similar tables 1B, 1C etc. for other given values of r and C .

TABLE 2
 Q from the resonance curve

Value of C (μF)	Value of r (ohm)	Resonant freq. f_0 from graph (Hz)	Bandwidth ($f_2 - f_1$) from graph (Hz)	$Q = \frac{f_0}{f_2 - f_1}$
...
...
...
etc.	etc.	etc.	etc.	etc.

Value of C
(μF)

...

etc.

Therefor

Add two
more
columns
to measure
 V_c and V_r

Take 3 sets
 $\sqrt{C R_1}$
 $\sqrt{C R_2}$
 $\sqrt{C R_3}$

Note : Fr
known from t

Using di
measuring in
relation

other values

to a chosen scale, and the segment With centre at B, at E. Then DE and current, and so the capacitor losses are current over V_c . the voltage across

Part 3 : EXPERIMENTS

TABLE 3

 Q from the ratio V_c/V_i at resonanceInput voltage $V_i = \dots$ volt.

Value of C (μF)	Value of r (ohm)	Resonant freq. f_0 from graph (Hz)	Voltage across the capacitor V_c (volt)	$Q = \frac{V_c}{V_i}$ (= Q_1 , say)	Q from Table 2 (= Q_2 , say)	Remarks
...	Q_1 and Q_2 are nearly equal
...	
...	
etc.	etc.	etc.	etc.	etc.	etc.	

TABLE 4

To draw the phasor diagram at resonance

A. Choice of scale for the phasor diagram

Resonant frequency $f_0 = \dots$ Hz.

1 cm represents ... volt.

Therefore, $V_i = \dots$ volt $\equiv \dots$ cm $= OA$, $V'_i = \dots$ volt $\equiv \dots$ cm $= OB$, $V_r = \dots$ volt $\equiv \dots$ cm $= OD$, $V_c = \dots$ volt $\equiv \dots$ cm $= DE$, and $V_x = \dots$ volt $\equiv \dots$ cm $= EB$.

Table 4
Impedances across
C and L
(do for set I only)

B. Inference from the phasor diagram

$\angle BDE$	$\angle DBE$	Inference
...	...	<ul style="list-style-type: none"> (i) I leads V_c by 90° showing that the capacitor is a good one. (ii) V_x leads I by ... which is less than 90°. So the inductor is imperfect.

Note : From the resonant frequency f_0 , the inductance L can be calculated if the capacitance C is known from the relationship

$$L = \frac{1}{4\pi^2 f_0^2 C} \quad \dots \text{(vi)}$$

Using different known capacitors, L can be found from which the mean L is determined. By measuring input voltage V to the LCR circuit at resonance, its resistance R can be found from the relation

$$R = \frac{V}{I} = \frac{V_r}{V_i} \quad \dots \text{(vii)}$$

* Plot Z_L vs f and Z_C vs f in a single graph paper

*Plot $1/Z_C$ vs f

Q is then found from

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

and compared with the values of Q obtained in TABLES 2 and 3.

The following table can be used for the above determination of L and Q .

TABLE 5
Determination of L and Q ($r = \dots$ ohm)

f_0 (from resonant curves) (Hz)	C (F)	L [from Eq. (vi)] (H)	Mean L (H)	Input voltage V (volt)	V_r (volt)	R [from Eq. (vii)] (ohm)	Q $\left(= \frac{1}{R} \sqrt{\frac{L}{C}}\right)$
...
...
etc.	etc.	etc.			etc.	etc.	etc.

Percentage Error in Q :

We have
$$Q = \left| \frac{V_c}{V_i} \right|$$

Hence, if δQ is the error in Q , we have

$$\frac{\delta Q}{Q} = \frac{\delta V_c}{V_c} + \frac{\delta V_i}{V_i}$$

where δV_c and δV_i are the smallest divisions of the scales used for measurements of V_c and V_i respectively. $\frac{\delta Q}{Q}$ is the proportional error; multiplying it by 100 we get the percentage error in Q .

Discussions :

1. The capacitance C must be much larger than the input capacitance C_i of the EVM.
2. The effect of the self-capacitance of the coil can be neglected over the frequency range of interest here.
3. Capacitors are more or less ideal while inductors are not. Hence the voltage is measured across the capacitor, and not across the inductor, to find Q .
4. The measured voltages are the effective or r.m.s. values.
5. If the source resistance R_s is not sufficiently small, the output voltage of the audio oscillator can be fed to a unity gain buffer. The output of the buffer supplies power to the given network. In this case, the effective source resistance becomes very small.
6. The connecting wires must be straight and short.
7. If the amplitude of the output voltage of the oscillator changes with frequency, it must be adjusted.

* from the slope of Z_L vs graph find L

* from the slope of $\frac{1}{Z_L}$ vs graph to find C

8. While voltage V_i should be Eq. (iii), be found.

10. The ac-
tance.

1. What is Ans. A the cur-
2. What is Ans. U
3. What is Ans. T resonan-
4. What is Ans. T ratio of circuit $(f_2 - f_1)$ ratio of All the
5. Why is Ans. T supply
6. What Ans. I at res indica-
the h-
The h-
7. What Ans. reson-
f₀ is
8. For Ans.
9. Wh Ans.
10. Wh Ans.